

PASS – Computer Systems

Week 4

1. Tips for Week 4 exam

- 1) Truly understand every question in the prac exam – what the right answer is and why.
- 2) Study the revision quiz (in MyUni module)
- 3) Review your notes, make sure you understand all the key concepts like canonical representation, binary representation (min, max, conversion, overflow), binary arithmetic, ALU, etc
- 4) Time yourself during the exam – e.g., 45 min for 25 questions → 1.8 min/question.

2. What is the smallest number of NOR gates required to implement an AND chip?

3

3. C++ has the following bitwise operators, & (and), | (or) and ~(not) and a left shift operator <<.

What is the decimal value of the expression, $(1 \ll 3 | 1 \ll 1)$, if all numbers are represented in 8-bit two's complement. Your answer must start with an initial sign, + or -. The rest of your answer must only contain decimal digits.

00001010 $0 + 2^1 + 0 + 2^3$
= 10

When shifting a signed value, the >> operator is an **arithmetic shift**. What is the decimal value of the expression, $(-128 \gg 3 | 1 \gg 1)$, if all numbers are represented in 8-bit two's complement. Your answer must start with an initial sign, + or -. The rest of your answer must only contain decimal digits.

+ 16

-128 : 1000 0000

>> 3 : 0001 0000

1771 : 00000000 OR = +16


4. Write down the canonical representation for the **sum** and **carry** output of the **HalfAdder** boolean function. (use !, &, + operators to represent not, and, or)

| a | b | sum | carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

| | |
|---------|-------------------------------------|
| Sum = | $\bar{a} \cdot b + a \cdot \bar{b}$ |
| Carry = | $a \cdot b$ |

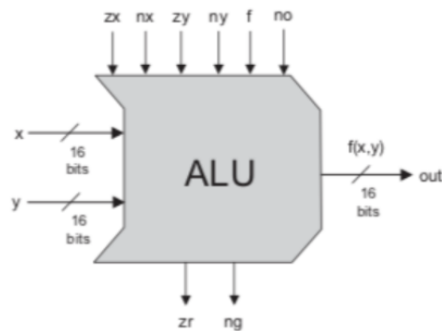5. ALU

The following diagram shows the interface to the Hack ALU and the effect of the six control inputs zx , nx , zy , ny , f and no .



| zx | nx | zy | ny | f | no |
|---|--|---|--|---|--|
| if $zx == 0$ then $x1 = x$ else $x1 = 0$ | if $nx == 0$ then $x2 = x1$ else $x2 = !x1$ | if $zy == 0$ then $y1 = y$ else $y1 = 0$ | if $ny == 0$ then $y2 = y1$ else $y2 = !y1$ | if $f == 0$ then $fout = x2 \& y2$ else $fout = x2 + y2$ | if $no == 0$ then $out = fout$ else $out = !fout$ |

Notes:


- The values of $x1$, $x2$, $y1$, $y2$, $fout$ and out must be expressed as simplified arithmetic expressions and may include a single x , a single y , a single digit (0, 1 or 2) and the operators, + and -.
- If an expression starts with -, all operators must be -.
- If an expression is 0, it may be expressed as 0 or zero.
- The values of zr and ng must be expressed as true or false.
- Your answers must not include any spaces.

What are the values $x1$, $x2$, $y1$, $y2$, $fout$ and out when the ALU control inputs have the following values?

| | | | |
|---|-------|------------------------------------|----|
| if zx == 0 then x1 = | x | , then if nx == 0 then x2 = | x |
| if zy == 1 then y1 = | 0 | , then if ny == 1 then y2 = | -1 |
| If f == 1 then fout = | x - 1 | | |
| If no == 0 then out = | x - 1 | | |
| What values would be output on the zr and ng wires if the values of x and y are as follows? | | | |
| If x == 1 and y == 2 then zr = | true | | |
| If x == 2 and y == 3 then ng = | false | | |

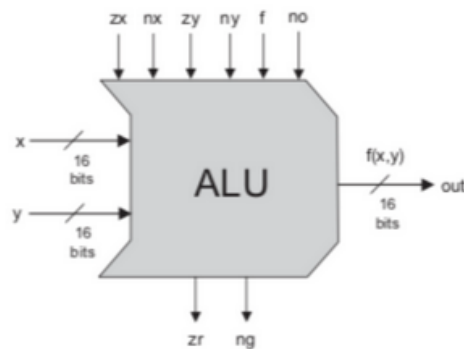6. Another ALU question

The following diagram shows the interface to the Hack ALU and the effect of the six control inputs zx , nx , zy , ny , f and no .



| zx | nx | zy | ny | f | no |
|---|--|---|--|---|--|
| if $zx == 0$ then $x1 = x$ else $x1 = 0$ | if $nx == 0$ then $x2 = x1$ else $x2 = !x1$ | if $zy == 0$ then $y1 = y$ else $y1 = 0$ | if $ny == 0$ then $y2 = y1$ else $y2 = !y1$ | if $f == 0$ then $fout = x2 \& y2$ else $fout = x2 + y2$ | if $no == 0$ then $out = fout$ else $out = !fout$ |

Notes:


- The values of $x1$, $x2$, $y1$, $y2$, $fout$ and out must be expressed as **true**, **false** or as simplified boolean expressions.
- Boolean expressions may include a single x , a single y and the operators $\&$, $|$ and $!$.
- The values of zr and ng must be expressed as **true** or **false**.
- Your answers must not include any spaces.

What are the values $x1$, $x2$, $y1$, $y2$, $fout$ and out when the ALU control inputs have the following values?

| | | | |
|---|-----------------|------------------------------------|----|
| if zx == 0 then x1 = | x | , then if nx == 0 then x2 = | x |
| if zy == 1 then y1 = | 0 | , then if ny == 1 then y2 = | -1 |
| If f == 0 then fout = | x f -1 | | |
| If no == 0 then out = | x f -1 | | |
| What values would be output on the zr and ng wires if the values of x and y are as follows? | | | |
| If x == true and y == false then zr = | x-1 = -1 false | | |
| If x == true and y == true then ng = | x-1 = -1 true | | |

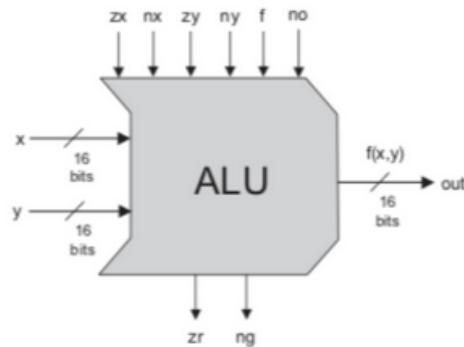7. More ALU

The following diagram shows the interface to the Hack ALU and the effect of the six control inputs zx , nx , zy , ny , f and no .



| zx | nx | zy | ny | f | no |
|---|--|---|--|---|--|
| if $zx == 0$ then $x1 = x$ else $x1 = 0$ | if $nx == 0$ then $x2 = x1$ else $x2 = !x1$ | if $zy == 0$ then $y1 = y$ else $y1 = 0$ | if $ny == 0$ then $y2 = y1$ else $y2 = !y1$ | if $f == 0$ then $fout = x2 \& y2$ else $fout = x2 + y2$ | if $no == 0$ then $out = fout$ else $out = !fout$ |

Notes:

- The values of $x1$, $x2$, $y1$, $y2$, $fout$ and out must be expressed as **true**, **false** or as simplified boolean expressions.
- Boolean expressions may include a single x , a single y and the operators $\&$, $|$ and $!$.
- The values of zr and ng must be expressed as **true** or **false**.
- Your answers must not include any spaces.

What are the values $x1$, $x2$, $y1$, $y2$, $fout$ and out when the ALU control inputs have the following values?

| | | | |
|---|-----------------|------------------------------------|---|
| if zx == 0 then x1 = | x | , then if nx == 0 then x2 = | x |
| if zy == 0 then y1 = | y | , then if ny == 0 then y2 = | y |
| If f == 0 then fout = | x & y | | |
| If no == 1 then out = | !x & !y | | |
| What values would be output on the zr and ng wires if the values of x and y are as follows? | | | |
| If x == true and y == false then zr = | 0 + 1 = 1 false | | |
| If x == true and y == true then ng = | 0 + 0 = false | | |